

Junchao Zhou, Chenhan Dai

EE469

April 5, 2023

Lab 1 Report

Procedure

This lab consisted of three tasks: design a simple module using Quartus, and do the same thing for a register file and design an Arithmetic Logic Unit ALU. Then simulate both of these approaches on ModelSim.

Task #1: Warmup Exercise on ModelSim

The first task is to install the Quartus 17.0 and ModelSim, and then apply a simulation on full adder.

Task #2: Register File

In this task, we built a 16 by 32 register file with two read ports, one write port and asynchronous. Which means there will be 16 addresses, each address storing 32 bits value. And the read port will reflect the value of the address without the influence of clock.

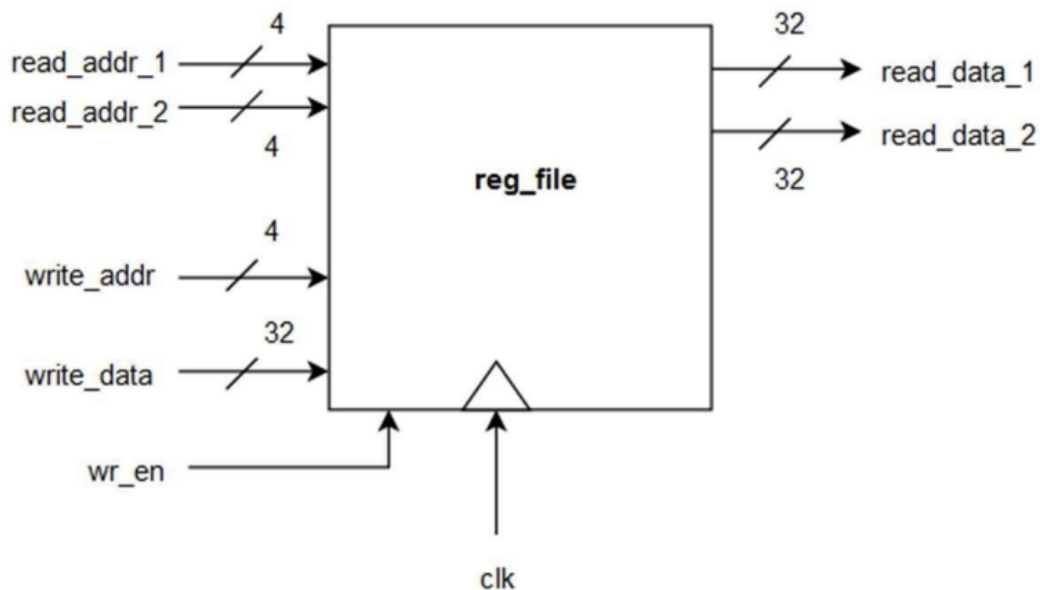


Figure 1: 16 by 32 register with two read port, one write port and asynchronous

Task #3: ALU

This task asks us to build an ALU (Arithmetic Logic Unit) which computes any of four operations: addition, subtraction, ANDing and ORing. It computes every operation and selects one result based on the control signals given in Figure 2. There are other 4-bit flags to see which conditions the result meets in Figure 3. The schematic diagram of ALU with flags is given in Figure 4.

ALU: Arithmetic Logic Unit

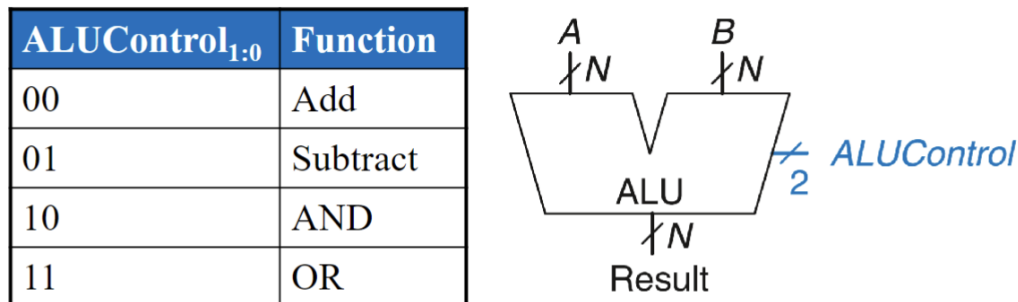


Figure 2: ALUControl and function

The four bits of ALUFlags should be TRUE if a condition is met. The four flags are as follows:

ALUFlag bit	Meaning
3	Result is negative
2	Result is 0
1	The adder produces a carry out
0	The adder results in overflow

Figure 3: ALU flags bit and meaning

 


Figure 5: Register file simulation diagram

Task 3:

According to the schematic diagram above, we built the ALU in Verilog. The testbench of ALU is based on the test listed in table 1. The simulation graphs are shown in figure 6 and fill the result from the figure into table 1.

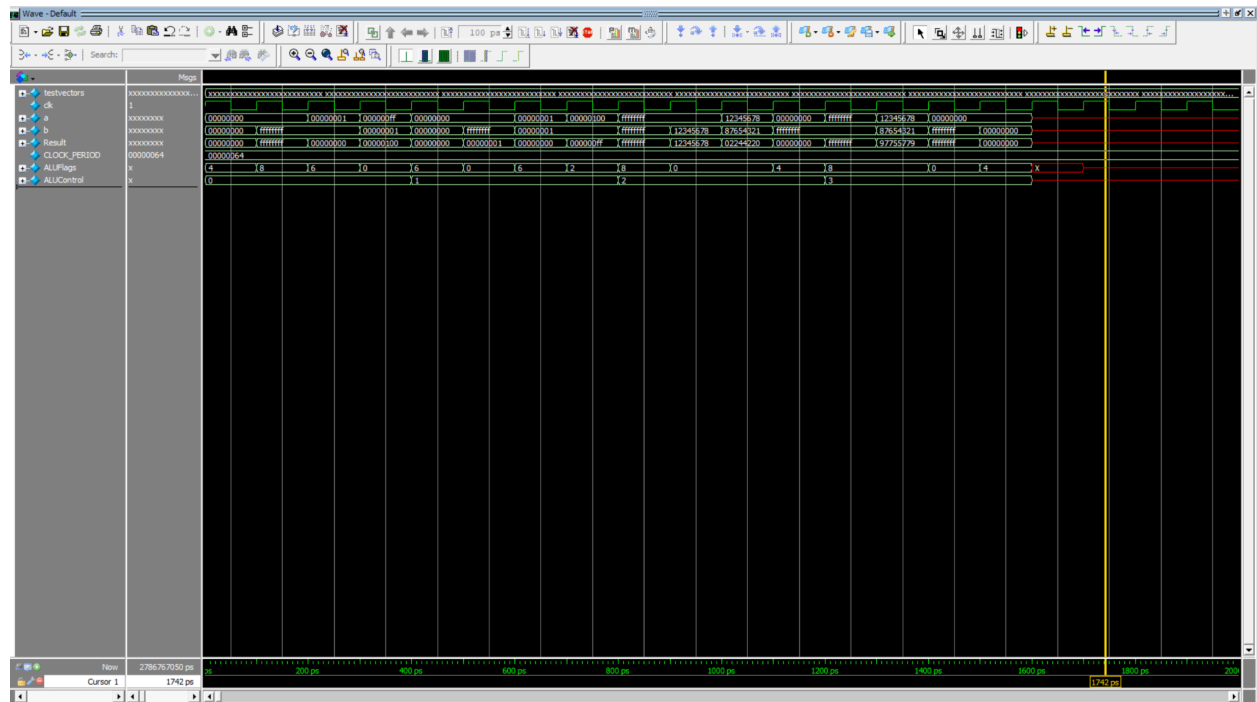


Figure 6: ALU simulation diagram

Test	ALUControl[1:0]	A	B	Result	ALUFlags
ADD 0+0	0	00000000	00000000	00000000	4
ADD 0+(-1)	0	00000000	FFFFFFFF	FFFFFFFF	8
ADD 1+(-1)	0	00000001	FFFFFFFF	00000000	6
ADD FF+1	0	000000FF	00000001	00000100	0
SUB 0-0	1	00000000	00000000	00000000	6
SUB 0-(-1)	1	00000000	FFFFFFFF	00000001	0
SUB 1-1	1	00000001	00000001	00000000	6
SUB 100-1	1	00000100	00000001	000000FF	2
AND FFFFFFFF, FFFFFFFF	2	FFFFFFFF	FFFFFFFF	FFFFFFFF	8
AND FFFFFFFF, 12345678	2	FFFFFFFF	12345678	12345678	0
AND 12345678, 87654321	2	12345678	87654321	02244220	0

AND 00000000, FFFFFFFF	2	00000000	FFFFFFFF	00000000	4
OR FFFFFFFF, FFFFFFFF	3	FFFFFFFF	FFFFFFFF	FFFFFFFF	8
OR 12345678, 87654321	3	12345678	87654321	97755779	8
OR 00000000, FFFFFFFF	3	00000000	FFFFFFFF	FFFFFFFF	0
OR 00000000, 00000000	3	00000000	00000000	00000000	4

Table 1. ALU operation

Appendix: SystemVerilog code

1) reg_file.sv

```
1 //Junchao Zhou, Chenhan Dai
2 //04/05/2023
3 //EE469
4 //Lab #1, Task2
5
6 //reg_file takes clk, wr_en, 32-bit write_data, 4-bit write_addr, read_addr1, read_addr2 as inputs,
7 // 32-bit read_data1, read_data2 as outputs. And we define a 16 * 32 bit memory.
8 // If write enable, the write data is be written into the write_address of the memory,
9 // and we read the data in read_addr1 and read_addr2 of the memory asynchronously.
10
11 module reg_file(input logic clk, wr_en,
12                 input logic [31:0] write_data,
13                 input logic [3:0] write_addr,
14                 input logic [3:0] read_addr1, read_addr2,
15                 output logic [31:0] read_data1, read_data2);
16
17     //logic [15:0][31:0] memory;
18     logic [31:0] memory [0:15];
19
20
21     // Write port
22     always_ff @(posedge clk) begin
23         if (wr_en)
24             memory[write_addr] <= write_data;
25     end
26
27     // Read Port 1
28     assign read_data1 = memory[read_addr1];
29
30     // Read Port 2
31     assign read_data2 = memory[read_addr2];
32 endmodule
33
34
35
36
```

```

36
37 // reg_file_testbench tests three cases
38 // 1. the write data is written into the register file the clock cycle after wr_en is asserted
39 // 2. Read data is updated to the register at an address the same cycle the address was
40 // provided
41 // 3. Read data is updated to write data at an address the cycle after the address was provided
42 // if the write address is the same and wr_en was asserted
43
44 module reg_file_testbench();
45 //Inputs
46 logic clk, wr_en;
47 logic [31:0] write_data;
48 logic [3:0] write_addr, read_addr1, read_addr2;
49
50 //Outputs
51 logic [31:0] read_data1, read_data2;
52
53 reg_file dut(.clk, .wr_en, .write_data, .write_addr,
54             .read_addr1, .read_addr2, .read_data1, .read_data2);
55
56 always #10 clk = ~clk;
57
58 // Initialize inputs
59 initial begin
60     clk = 0;
61     wr_en = 0;
62     write_data = 0;
63     write_addr = 0;
64     read_addr1 = 0;
65     read_addr2 = 1;
66     #10;
67
68     // Write data is written the cycle after wr-en is asserted
69     wr_en = 0;
70     write_addr = 0;
71     write_data = 32'h00abcdef;
72     #10;
73
74     wr_en = 1; #20;
75
76     // Read data is updated the same cycle the address is provided
77     wr_en = 0;
78     write_data = 32'h11111111;
79     write_addr = 1;
80     #10;
81
82     wr_en = 1;
83     #10;
84
85
86     read_addr1 = 0;
87     read_addr2 = 1;
88     #10;
89
90
91     // Read data is updated the cycle after the address is provided and
92     // wr_en is asserted
93     write_data = 32'h22222222;
94     write_addr = 0;
95     wr_en = 0;
96     #10;
97
98     wr_en = 1;
99     #10;
100
101     read_addr1 = 0;
102     read_addr2 = 1;
103     #10;
104     $stop;
105 end
106
107 endmodule

```

2) alu.sv


```

1 //Junchao Zhou, Chenhan Dai
2 //04/05/2023
3 //EE469
4 //Lab #1, Task2
5
6 // alu take 32-bit a, b, 2-bit ALUControl as input and return 32-bit Result and 4-bit ALUFlags as
7 // outputs. We define a 32-bit n-b as the inverse of b and a 33-bit temp to find if the ALU has
8 // carryout.
9 module alu(input logic[31:0]a, b,
10           input logic[1:0] ALUControl,
11           output logic[31:0] Result,
12           output logic[3:0] ALUFlags);
13
14     logic[31:0] n_b;
15     logic[32:0] temp;
16     assign n_b = ~b;
17
18     always_comb begin
19       case(ALUControl)
20         2'b00: begin
21           Result = a + b;
22           temp = a + b;
23         end
24         2'b01: begin
25           Result = a - b;
26           temp = a + n_b + 1;
27         end
28         2'b10: begin
29           Result = a & b;
30           temp = 0;
31         end
32         2'b11: begin
33           Result = a | b;
34           temp = 0;
35         end
36       endcase
37
38       // ALUFlags[0] = 1 when the adder results in overflow
39       ALUFlags[0] = ~(a[31] ^ b[31] ^ ALUControl[0]) & (a[31] ^ Result[31]) & ~ALUControl[1];
40       //ALUFlags[0] = (~Result[31] & a[31] & ~b[31])|(Result[31]&~a[31] &~b[31]);
41
42       // ALUFlags[1] = 1 when the adder produces a carry out
43       ALUFlags[1] = temp[32];
44
45       // ALUFlags[2] = 1 when the result is 0
46       ALUFlags[2] = Result == 0;
47
48       // ALUFlags[3] = 1 when the result is negative
49       ALUFlags[3] = Result[31];
50     end
51 endmodule
52

```

```

54
55 // alu_testbench read the vector file alu.tv and tests all the cases in the file
56 module alu_testbench();
57   logic [31:0]a, b;
58   logic [1:0] ALUControl;
59   logic [31:0] Result;
60   logic [3:0] ALUFlags;
61   logic clk;
62   logic [103:0] testvectors [1000:0];
63
64   alu dut (.a(a), .b(b), .ALUControl(ALUControl), .Result(Result), .ALUFlags(ALUFlags));
65
66   parameter CLOCK_PERIOD = 100;
67
68   initial clk = 1;
69   always begin
70     #(CLOCK_PERIOD/2);
71     clk = ~clk;
72   end
73
74   initial begin
75     $readmemh("alu.tv", testvectors);
76
77     for(int i = 0; i < 20; i = i + 1) begin
78       {ALUControl, a, b, Result, ALUFlags} = testvectors[i]; @(posedge clk);
79     end
80   end
81 end
82 endmodule
83
84
85

```

3)alu.tv

1	0_00000000_00000000_00000000_4
2	0_00000000_FFFFFFFF_FFFFFFFF_8
3	0_00000001_FFFFFFFF_00000000_6
4	0_000000FF_00000001_00000100_0
5	1_00000000_00000000_00000000_6
6	1_00000000_FFFFFFFF_00000001_0
7	1_00000001_00000001_00000000_6
8	1_00000100_00000001_000000FF_2
9	2_FFFFFFFF_FFFFFFFF_FFFFFFFF_8
10	2_FFFFFFFF_12345678_12345678_0
11	2_12345678_87654321_02244220_0
12	2_00000000_FFFFFFFF_00000000_4
13	3_FFFFFFFF_FFFFFFFF_FFFFFFFF_8
14	3_12345678_87654321_97755779_8
15	3_00000000_FFFFFFFF_00000000_0
16	3_00000000_00000000_00000000_4